

Transmission Line Simulator
 H. Johnson, 5/29/95
 file: shortlin.mcd

Investigation of unterminated lines showing effects of rise time and line length.
 Order of operations: Establish indices for FFT operations, generate frequency response of unterminated line, convert to time domain waveform and display.

Establish indices for FFT operations

Sampling resolution, in seconds	$\Delta T := 10^{-10}$	
	$f_{\text{sample}} := \frac{1}{\Delta T}$	
Desired trace length, in seconds	$T_{\text{len}} := 100 \cdot 10^{-9}$	
	$\log N := \text{ceil} \left(\frac{\log \left(\frac{T_{\text{len}}}{\Delta T} \right)}{\log(2)} \right)$	
Pick next biggest power of two trace length	$N := \text{floor} \left(2^{\log N + 0.5} \right)$	
Index to time points	$j := 0, 1 \dots N - 1$	
Index to frequency points	$k := 0, 1 \dots \frac{N}{2}$	
List of frequency points	$f_k := f_{\text{sample}} \cdot \frac{k}{N}$	
	$s := 2j \cdot \pi \cdot f$	
Dummy vector used to vectorize some scalar functions	$V_{\text{dummy}_k} := 1$	
Vector operations	$\text{mpy}(A, B) := \overrightarrow{(A \cdot B)}$	$\text{div}(A, B) := \frac{\overrightarrow{A}}{B}$
Source impedance	$Z_S := 30$	$RL := 10000$
Load impedance	$Z_L(\text{cl}) := \text{div}(RL, 1 + s \cdot RL \cdot \text{cl})$	$\text{cl} = \text{load capacitance}$
Transmission line impedance	$Z_C := 65$	
Delay function, argument t is delay in seconds	$D(t) := \overrightarrow{\exp(-s \cdot t)}$	

Generate frequency response of unterminated line

Transmission line response (delay only, assume no distortion)

$$H(t) := D(t)$$

Acceptance function

$$A := \text{div}(ZC, ZS + ZC)$$

Near-end reflection

$$R1 := 1 - 2 \cdot A$$

Transmission function at far end

$$T(\text{cl}) := \text{div}(2 \cdot ZL(\text{cl}), ZL(\text{cl}) + ZC)$$

Far-end reflection

$$R2(\text{cl}) := T(\text{cl}) - 1$$

System response

$$S3(t, \text{cl}) := \text{div}(\text{mpy}(A, \text{mpy}(H(t), T(\text{cl}))), 1 - \text{mpy}(\text{mpy}(R2(\text{cl}), H(t)), \text{mpy}(R1, H(t))))$$

Driving waveform (a rectangular waveform, N/2 points in length)

$$S1_k := \text{if} \left(k = 0, \frac{N}{2}, \frac{1 - e^{-s_k \cdot \frac{N}{2} \cdot \Delta T}}{1 - e^{-s_k \cdot \Delta T}} \right) \cdot \frac{1}{\text{fsample}}$$

Linear rise/fall slopes;
0-100% risetime = r

$$\text{linear}(\mu, r) := \text{if} \left(\mu = 0, 1, \frac{1 - e^{-\mu \cdot r}}{1 - e^{-\mu \cdot \Delta T}} \cdot \frac{\Delta T}{r} \right)$$

Gaussian rise/fall slopes,
10-90% risetime = r

$$\text{gaussian}(\mu, r) := \text{if} \left[|\mu \cdot r| < 10, e^{\frac{\mu^2 \cdot \left(\frac{r}{2.56}\right)^2}{2}}, 0 \right] \cdot e^{-\mu \cdot \frac{r}{2}}$$

Use linear or gaussian slope

$$S2(r) := \xrightarrow{\hspace{1cm}} \text{gaussian}(s, r)$$

Convert to time domain and display

Ideal driving waveform

$$\text{SYS1} := \text{IFFT}(S1) \cdot \frac{\text{fsample}}{N}$$

Driving waveform with rise/fall slopes

$$\text{SYS2}(r) := \text{IFFT}(\text{mpy}(S1, S2(r))) \cdot \frac{\text{fsample}}{N}$$

Response of driven trace

$$\text{SYS3}(d, r, \text{cl}) := \text{IFFT}(\text{mpy}(\text{mpy}(S1, S2(r)), S3(d, \text{cl}))) \cdot \frac{\text{fsample}}{N}$$


Set nominal transmission line delay and risetime

$$\text{delay} := 10^{-9} \quad ZS = 30 \quad RL = 1 \times 10^4$$

risetime := 2·delay ZC = 65 CL := 0

Scale both delay and risetime to see
what happens

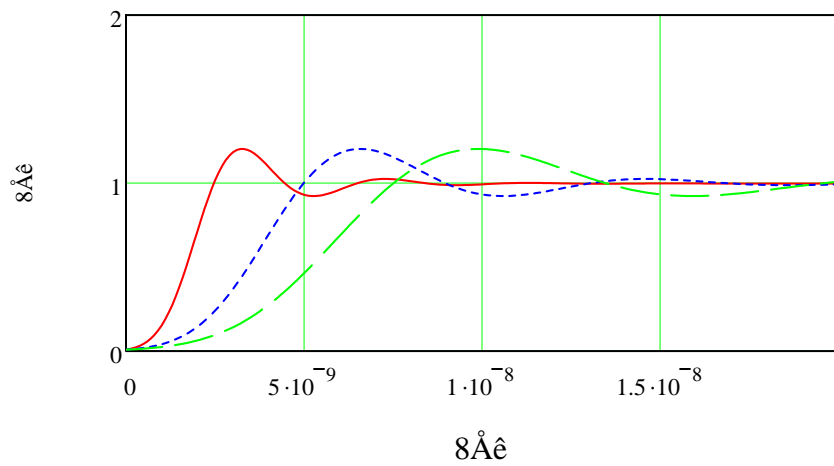X1 := SYS3(delay,risetime,CL)
X2 := SYS3(delay·2,risetime·2,CL)
X3 := SYS3(delay·3,risetime·3,CL)




Sample some test functions

X0 := SYS3(delay,0,CL)
X01 := SYS3(delay,delay,CL)
X02 := SYS3(delay,delay·2,CL)
X03 := SYS3(delay,delay·3,CL)
X04 := SYS3(delay,delay·4,CL)
X05 := SYS3(delay,delay·5,CL)
X06 := SYS3(delay,delay·6,CL)


Unterminated line response
Risetime set to 0, 2 and 3 times transmission line delay

ZS = 30 RL = 1×10^4
ZC = 65 CL = 0

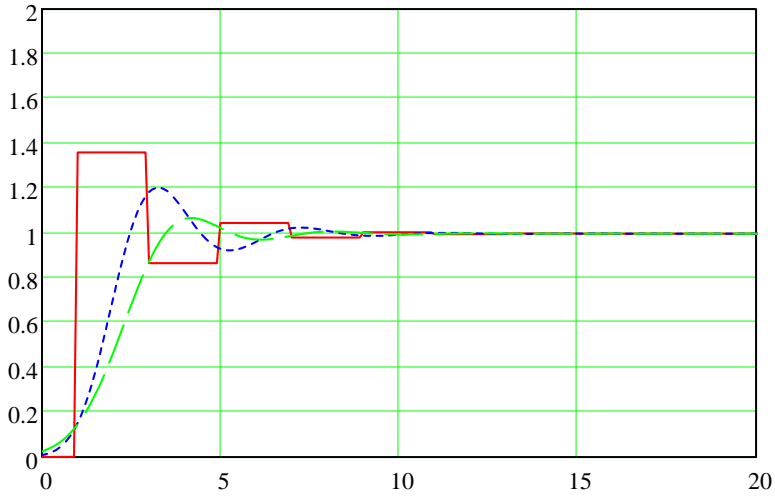


Unterminated line response
Risetime set to 4, 5 and 6 times transmission line delay

ZS = 30 RL = 1×10^4
ZC = 65 CL = 0

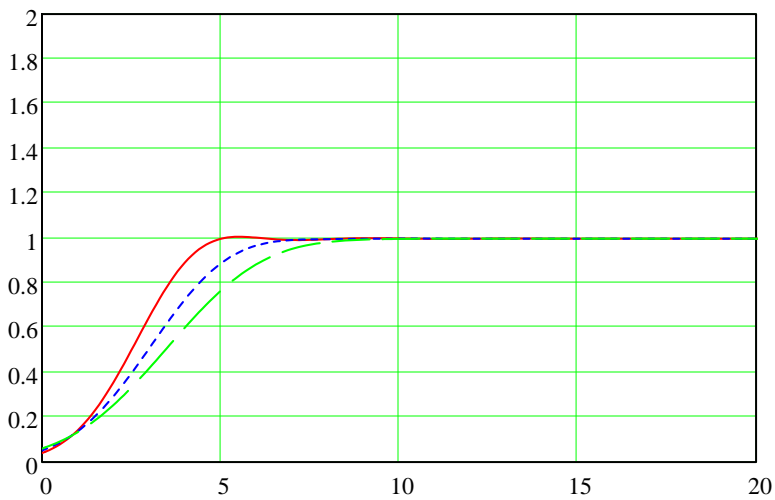

Underterminated line response
Risetime set to 4, 5 and 6 times transmission line delay
BLOWUP of vertical axis

ZS = 30 RL = 1×10^4
ZC = 65 CL = 0

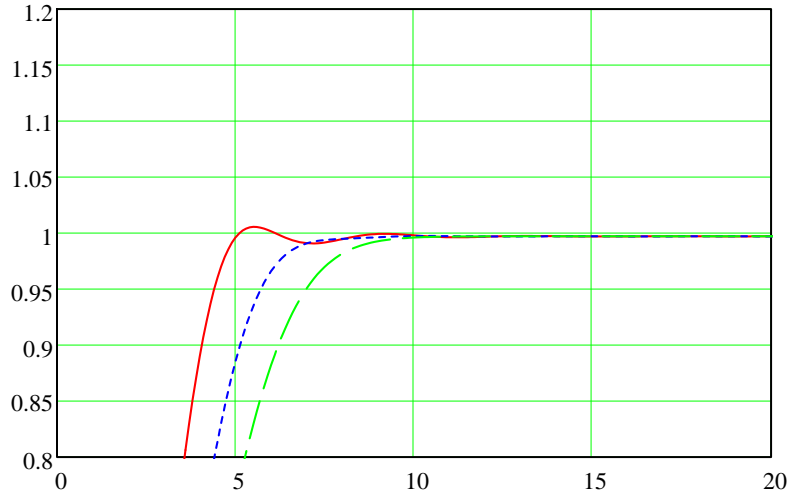

Investigate effect of termination capacitance

Set nominal transmission line delay and risetime

delay := $.5 \cdot 10^{-9}$ ZS = 30 RL = 1×10^4
risetime := 6 · delay ZC = 65

NOLOAD := 0

TEN_PF := $10 \cdot 10^{-12}$

TWENTY_PF := $20 \cdot 10^{-12}$


Adjust load capacitance and produce step response for each case

X1 := SYS3(delay,risetime,NOLOAD)

X2 := SYS3(delay,risetime,TEN_PF)

X3 := SYS3(delay,risetime,TWENTY_PF)

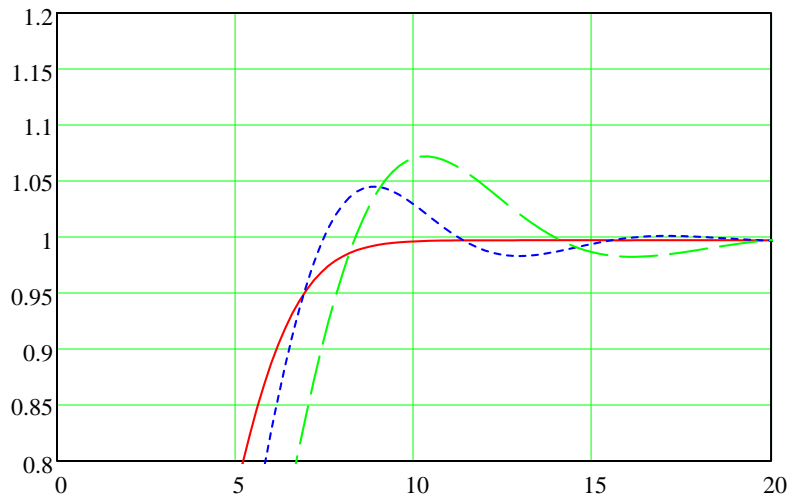Step response of 1/2 ns line with 0, 10 and 20 pF load
BLOWUP of vertical axis




Record frequency response for each value of load capacitance

Y1 := S3(delay, NOLOAD)

Y2 := S3(delay, TEN_PF)

Y3 := S3(delay, TWENTY_PF)

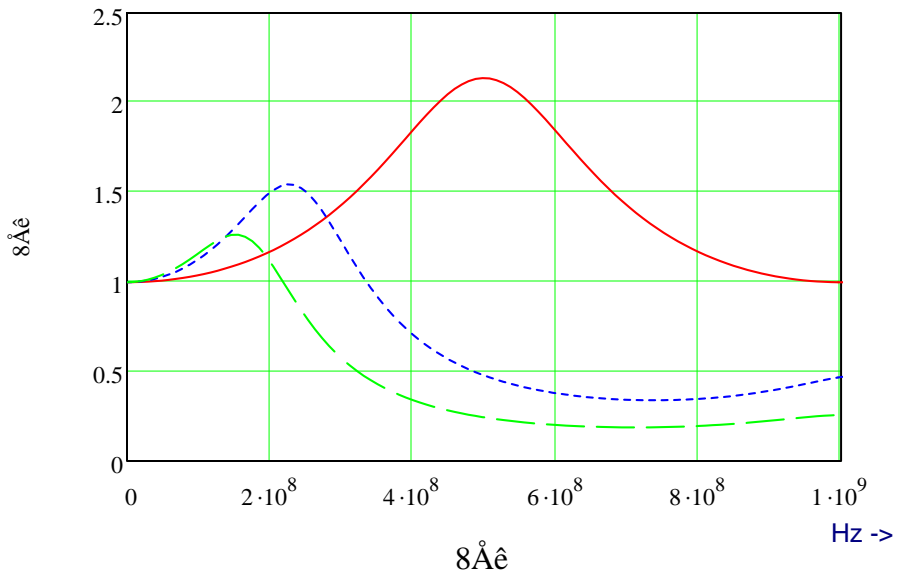Frequency response of 1/2 ns line with 0, 10 and 20 pF load



- Frequency
- - - Frequency
- - - Frequency

Knee frequency of driving waveform is 160 MHz (3-ns rise/fall time)

